

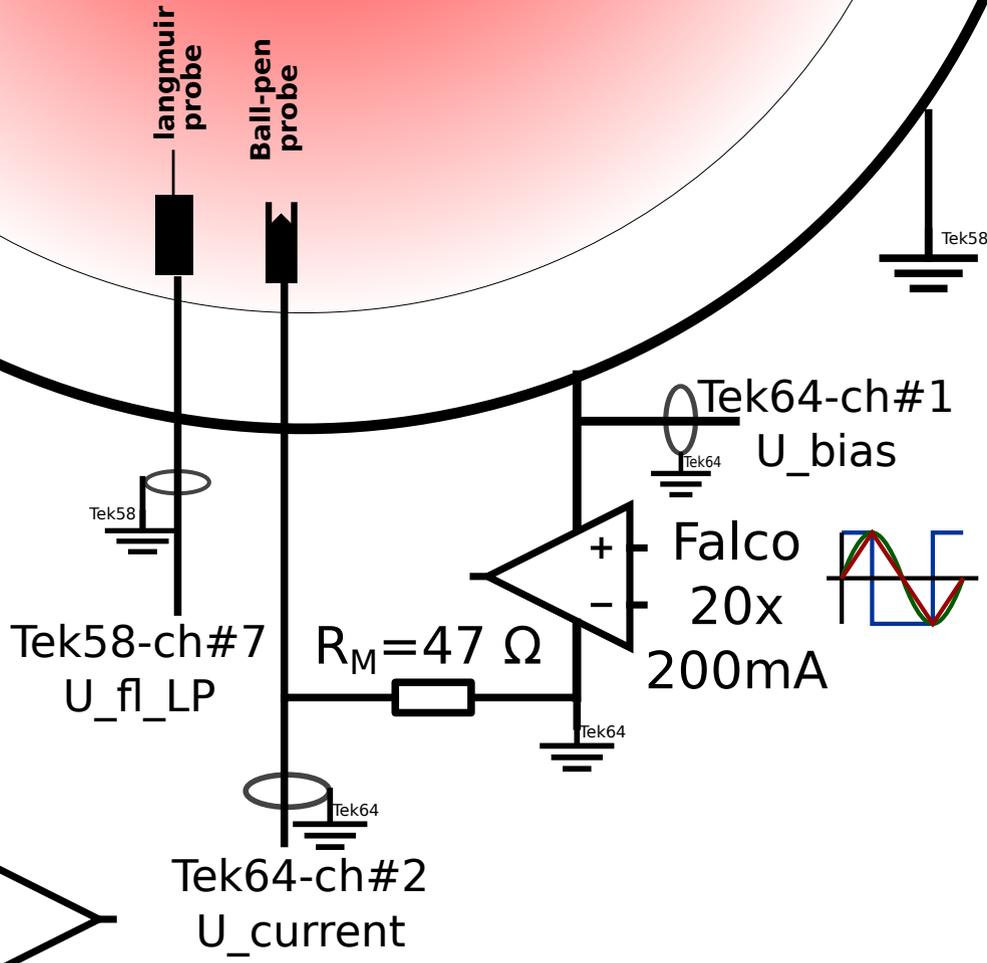
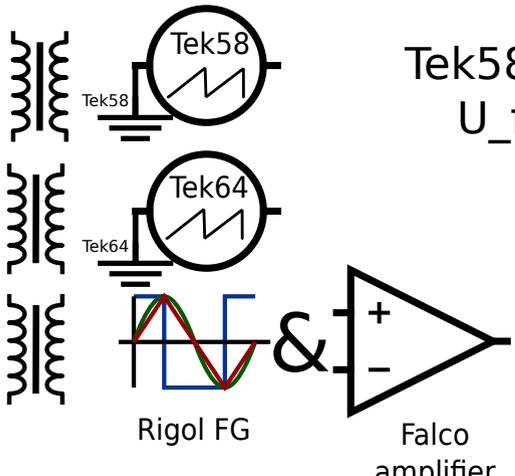
$$I_{\text{probe}} = (U_{\text{current}}) / R_M$$

(Tek64 -math#1)

$$U_{\text{probe}} = U_{\text{current}} + U_{\text{bias}}$$

(Tek64 -math#2)

Electrical grid

Function Generator  
RIGOL  
 $u_{fg}, f_{fg}$

